

UNIT-4

1. (A).What is code convertor? Explain its Working.
(b).What do you mean by combinational Circuit? Design the Half Adder using NAND Gate.
2. Explain the working of Comparator.
(b).What is Decoder? Explain and design BCD to Decimal Decoder.
3. i. explain 7-segment display
ii. differentiate between encoder and decoder?
- i. Differentiate between multiplexer and demultiplexer.
ii. Draw the logic diagram of half adder.
4. What is multiplexer? Explain all types of multiplexer by using an example.
5. Explain half subtractor
 - c. What is decoder? Design 5*32 decoder with the help of 3*8 decoder.
 - d. Design 4:1 multiplexer
 - e. Make 8421 to 2421 code converter
 - f. Explain full adder using k- map
 - g. Design 10 to 4 line encoder
 - h. Make 4 to 10 line decoder
 - i. Make code convertor from 8421 to cyclic
 - j. Design comparator for 2 bits
 - k. Make full adder